


# **EE338L Final Project**

**Design and Simulation of a Low-Power Two-Stage  
Operational Transconductance Amplifier**

**Rounok Joardar**


University of Texas, Austin  
Fall 2014 Prof. Nan Sun

# Two Stage OTA Design

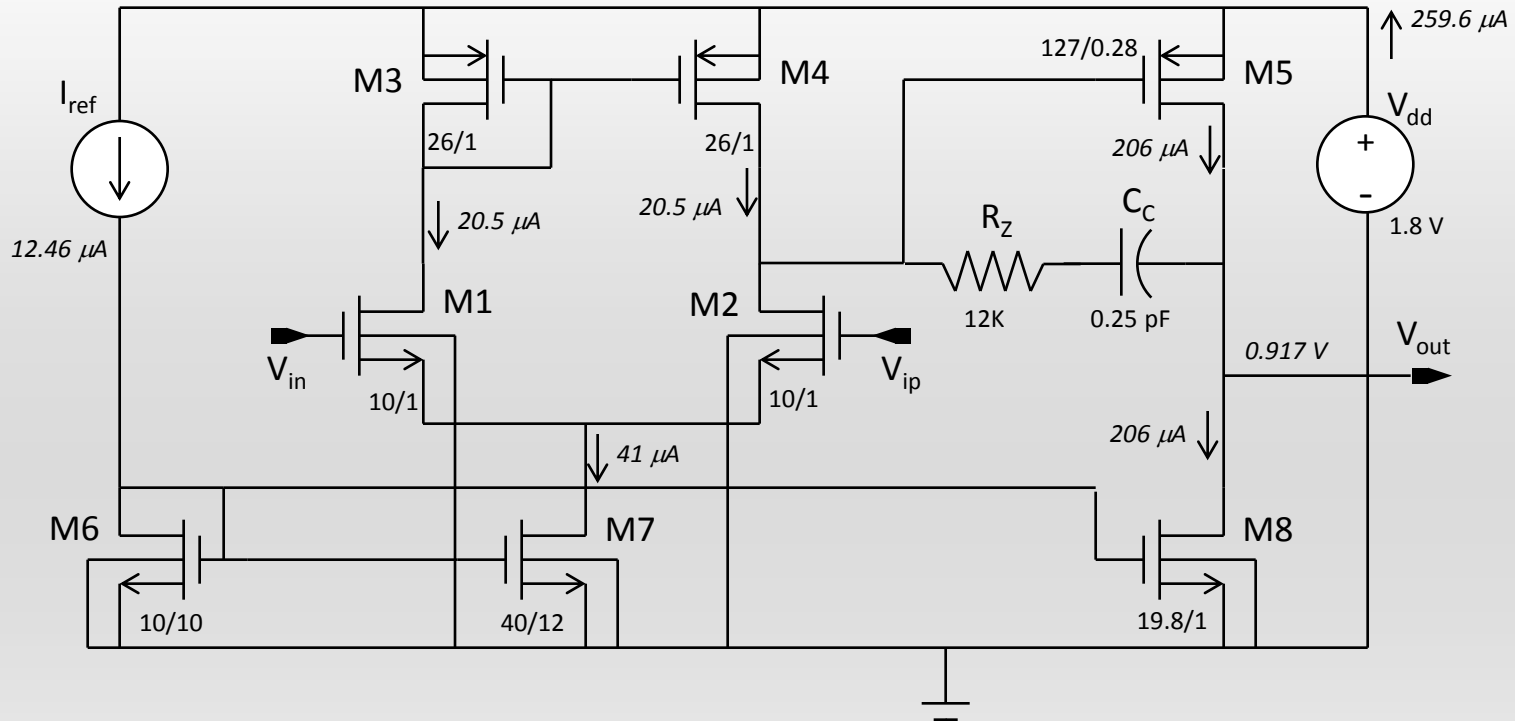

- Advantages compared to cascoded or telescopic differential stages
  - Lower power consumption of only 0.467mW
  - Simpler design allows for analytical debugging
- Larger MOSFET length (L = 1μm) reduces random mismatch and improves offset

# Design Strategy

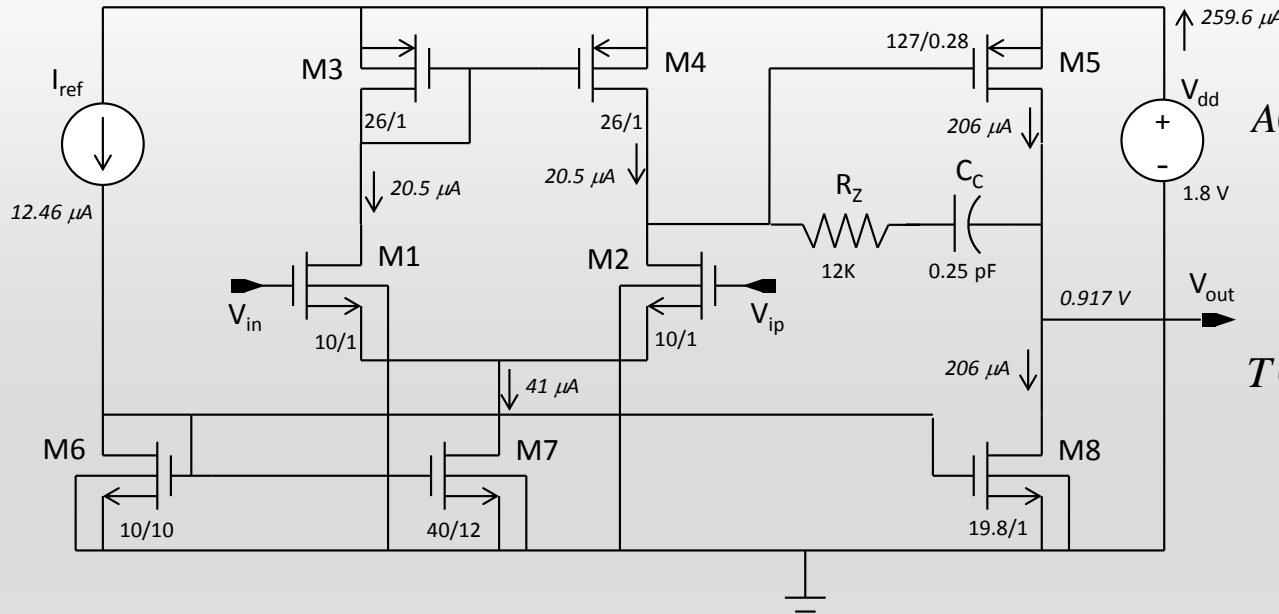

$$A(s) = A_{v0} \frac{\left(1 - \frac{s}{z_1}\right)}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right)}$$

$$T(s) = \frac{\beta A_{v0}}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right)}$$




- Circuit elements (sizes, biases, etc.) are chosen such that the zero cancels pole  $p_3$ 
  - Result is a two-pole loop gain expression
  - Manageable analytical expressions for unity gain frequency and phase margin
  - Compensation capacitor  $C_c$  results in "pole splitting"
  - Nulling resistor results in LHP zero and allows pole-zero cancellation

# Simulation Results

	Specification	From Theory	Final Design
DC small-signal gain	> 70 dB	74.9 dB	74.25 dB
Input-referred offset	< 10 $\mu\text{V}$	n/a	-1.6 $\mu\text{V}$
Input $V_{\text{cm}}$ range	[0.75, 1.05]	n/a	[0.75, 1.05]
Output swing	[0.3, 1.5]	n/a	[0.275, 1.56]
Unity gain frequency	> 100 MHz	90 MHz	101 MHz
Phase margin	> 45°	67.4°	55°
Power Consumption	< 1 mW	0.54 mW	0.467 mW
Settling time	Up	< 40ns	22 ns
	Down	< 40ns	32.4 ns
CMRR at DC	> 70 dB	76.4 dB	70.35 dB
PSRR at DC	> 70 dB	n/a	76.8 dB



- Paper design completed as first phase of project
- Initial paper design was reasonably close to target (with known exception of  $\omega_u$ )
- In second phase design was tuned to final targets using Spice
  - Phase margin sacrificed for unity gain frequency
  - Reference current reduced by pushing current mirror ratios to max limits

# Adjusting Unity Gain Frequency

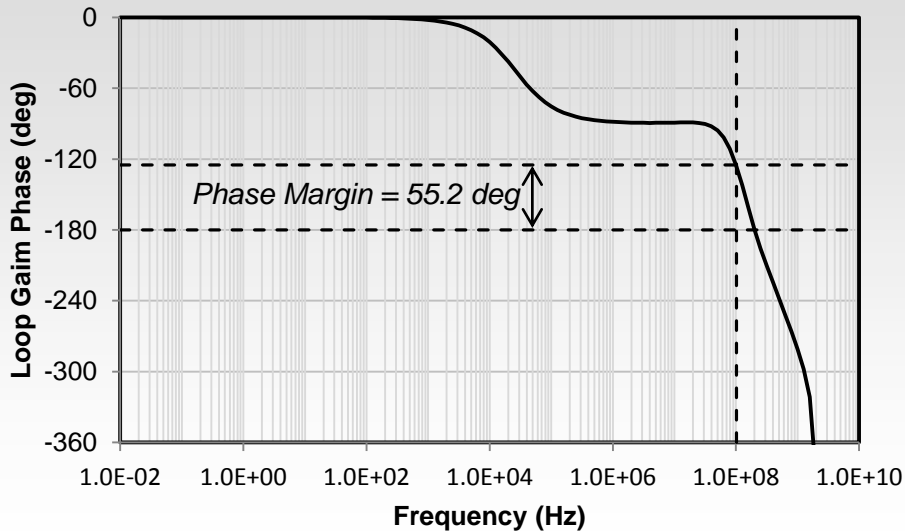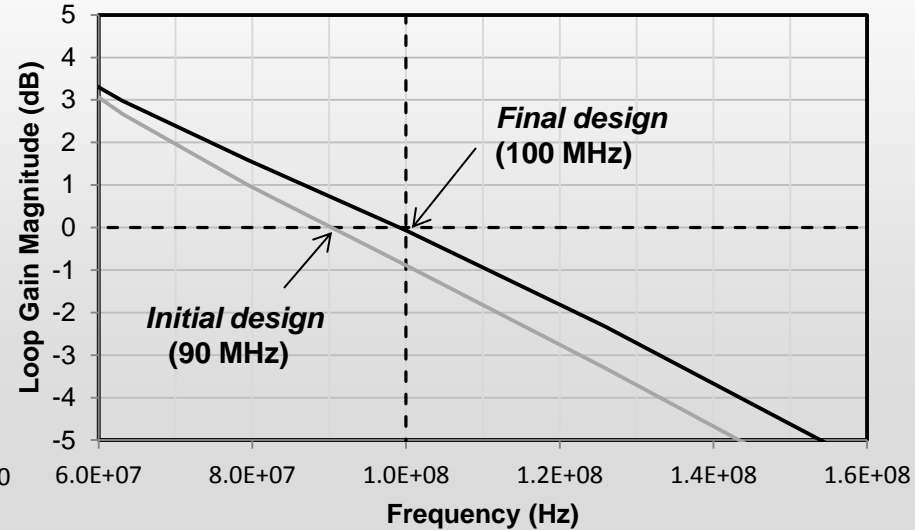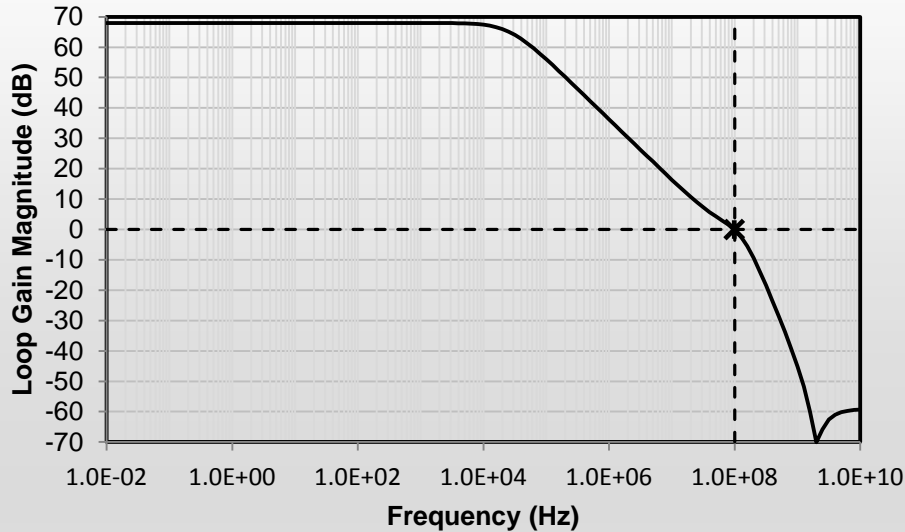

- Loop gain characteristics for initial theoretical design and final design are shown
- Initial design was a little short of target unity gain frequency
  - *Corrected by adjusting  $R_z$*
- Final design met both unity gain frequency and phase margin targets

# Settling Time

 
 


## Upward Input Step

## Downward Input Step

- Settling time characteristics adequately meet specifications in both directions
- Shows ringing behavior as expected from theory
  - Frequency of ringing is close to theoretically calculated value
- Upward step input settling time higher in Spice than in theory
  - Probably due to approximations made regarding the various capacitances and assuming the system to be linear

# Effect of Compensation Circuit

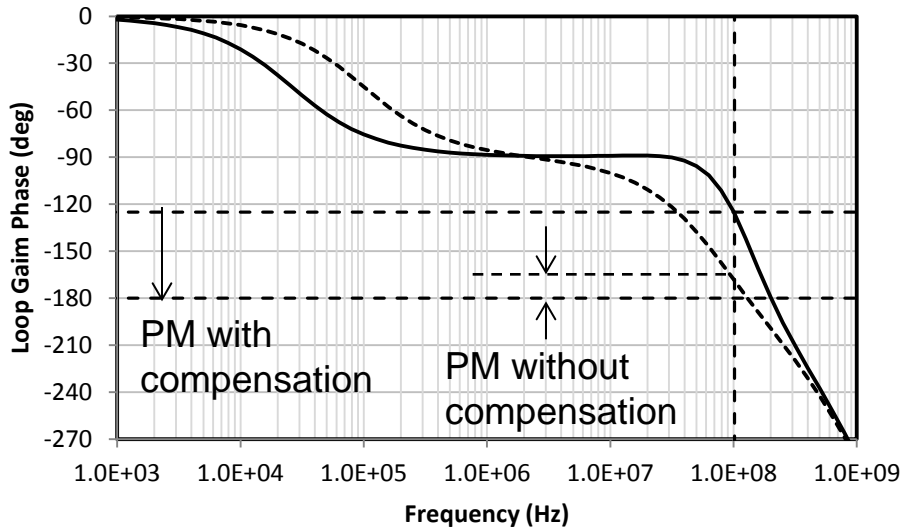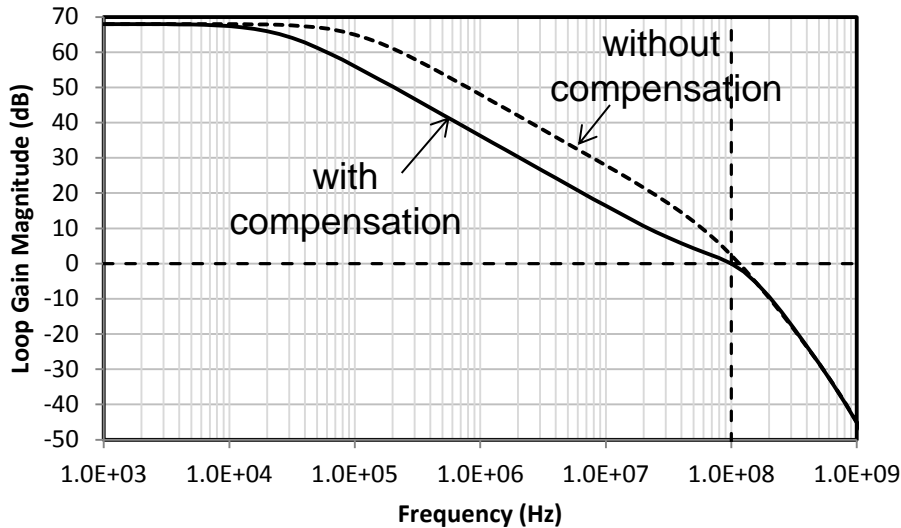

- Loop gain characteristics for final design are shown with and without the compensation capacitor and nulling resistor
- Not much effect on unity gain frequency (slight zero observable)
- Significant improvement on phase margin with compensation circuit